

Parishram (2025)

Physics


DPP: 5

Current Electricity

- Q1** A wire of resistance $12\ \Omega$ per metre is bent to form a complete circle of radius 10 cm. The resistance between any two of diametrically opposite points A and B as shown in the figure is:



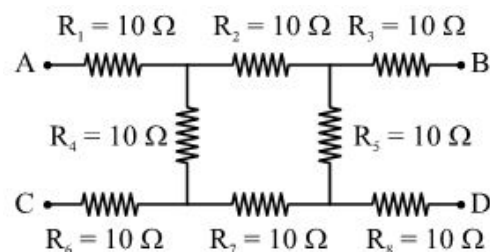
- (A) $3\ \Omega$
 (B) $6\ \Omega$
 (C) $6\pi\ \Omega$
 (D) $0.6\pi\ \Omega$
- Q2** Two wires of the same metal have same length, but their cross-sections are in the ratio 3 : 1. They are joined in series. The resistance of thicker wire is $10\ \Omega$. The total resistance of the combination will be:
 (A) $5/2\ \Omega$
 (B) $40/3\ \Omega$
 (C) $40\ \Omega$
 (D) $100\ \Omega$
- Q3** Three resistances each of $4\ \Omega$ are connected to form a triangle. The resistance between any two terminals is
 (A) $12\ \Omega$
 (B) $2\ \Omega$
 (C) $6\ \Omega$
 (D) $8/3\ \Omega$
- Q4** What will be the equivalent resistance between the points A and D?



- (A) $10\ \Omega$
 (B) $20\ \Omega$
 (C) $1.95\ \Omega$
 (D) $2\ V$

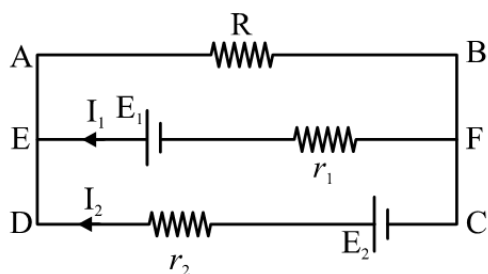
- Q5** The internal resistance of a cell of e.m.f. 2V is $0.1\ \Omega$. It is connected to a resistance of $3.9\ \Omega$. The voltage across the cell will be :
 (A) 0.5 V (B) 1.5 V
 (C) 1.95 V (D) 2 V
- Q6** For a cell, the terminal potential difference is 2.2 V, when circuit is open and reduces to 1.8 V, when cell is connected to a resistance $R = 5\ \Omega$. The internal resistance of cell (r) is
 (A) $10/9\ \Omega$
 (B) $9/10\ \Omega$
 (C) $11/9\ \Omega$
 (D) $5/9\ \Omega$
- Q7** Which of the following equations is a correct equation for the electrical circuit shown in the figure?






- (A) $E_2 - I_2 r_2 - E_1 - I_1 r_1 = 0$
 (B) $-E_2 - (I_1 + I_2) R + I_2 r_2 = 0$
 (C) $E_1 - (I_1 + I_2) R + I_1 r_1 = 0$
 (D) $E_1 - (I_1 + I_2) R - I_1 r_1 = 0$

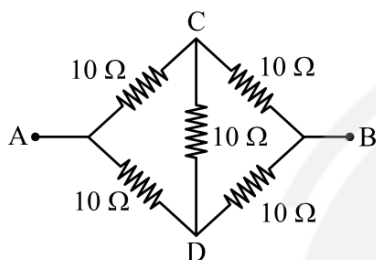Q8 The effective resistance between points A and B in the given circuit A is



- (A) 10Ω
 (B) 20Ω
 (C) 40Ω
 (D) 50Ω

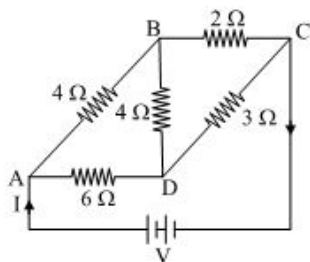Q9 For the network shown in the figure, the value of the current I is:



- (A) $9V/35$ (B) $18 V/5$
 (C) $5V/9$ (D) $5V/18$

Q10 The resistance of each arm of a Wheatstone bridge is 10Ω . A resistance of 10Ω is connected in series with the galvanometer. Then, the

equivalent resistance of the bridge across the battery will be:

- (A) 10Ω (B) 15Ω
 (C) 20Ω (D) 40Ω



Answer Key

Q1 (C)

Q2 (C)

Q3 (D)

Q4 (C)

Q5 (C)

Q6 (A)

Q7 (D)

Q8 (A)

Q9 (D)

Q10 (A)



[Android App](#)



[iOS App](#)



[PW Website](#)

